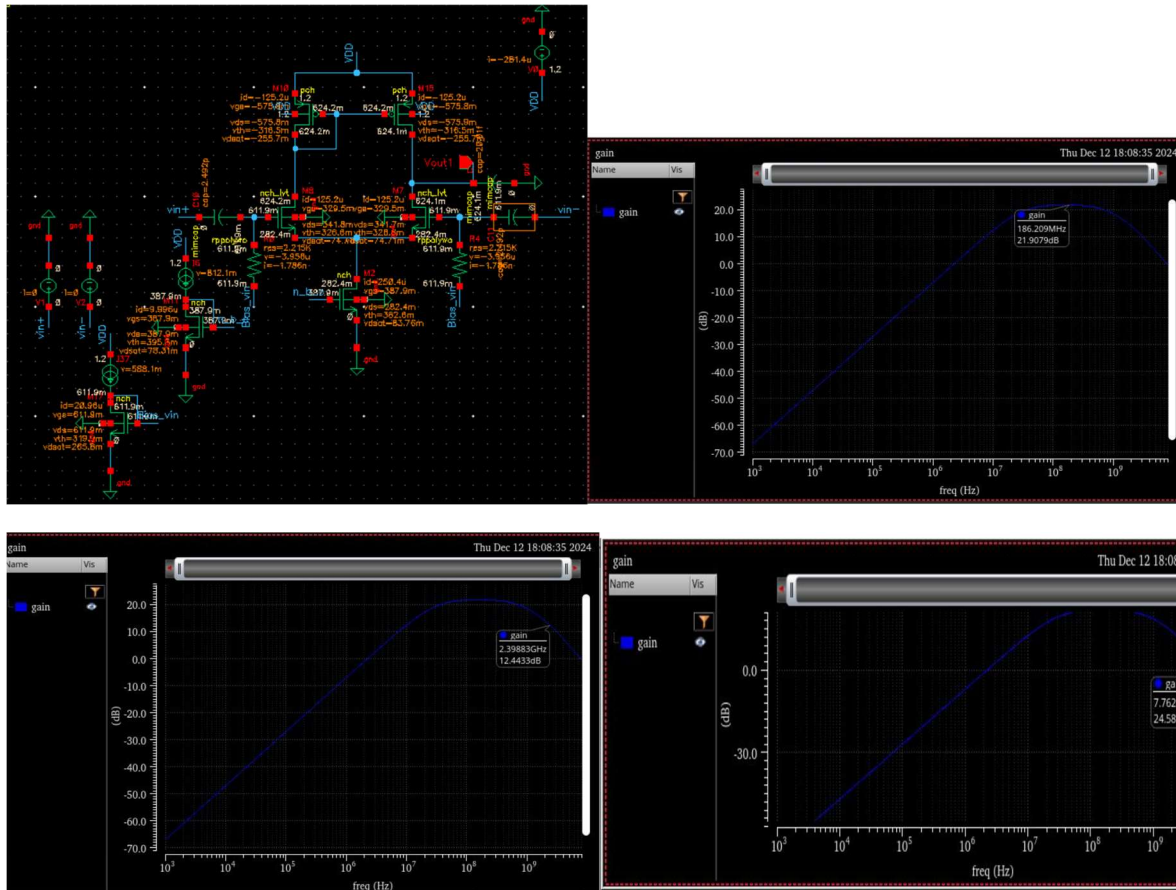



Final Project

Q1.



	Real	Specifications
Power Consumption	313.68 μ W	< 500 μ W
Gain at DC	21.9 dB	> 15 dB
Gain at 2.4GHz	12.4 dB	> 10 dB
Unity Gain Freq	7.76GHz	> 7.2GHz
DC Check (Saturation Status of All Transistors)	Yes	Yes

Layout

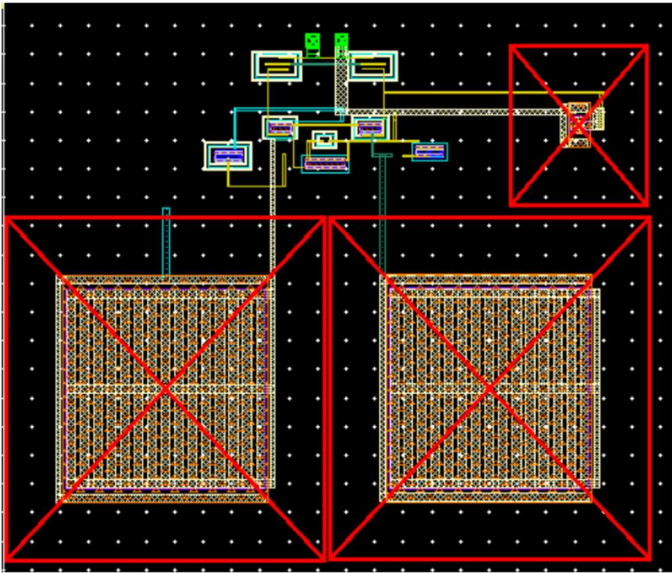


JKLibrary:Electronics2_Final::layout				
Cell/Rule	Hier	Top	Cells	Rules
Show: [Icons] Explain Return On Top				
Cell/Rule	Color	Count	Level	Status
TOP Electronics2_Final		39	0	
DRM.R.1		1		
LUP.6		24		
M1.DN.1		1		
M2.DN.1		1		
M3.DN.1		1		
M4.DN.1		1		
M5.DN.1		1		
M6.DN.1		1		
M7.DN.1		1		
M8.DN.5:L		1		
M9.A.1		2		
M9.DN.2		1		
OD.DN.2		1		
PO.DN.2		1		
RPO.A.1		1		
				Cell/Rule
				1 Electronics2_Final/M1.DN.1

No DRC Error

2 LVC Errors Detected

Q2.

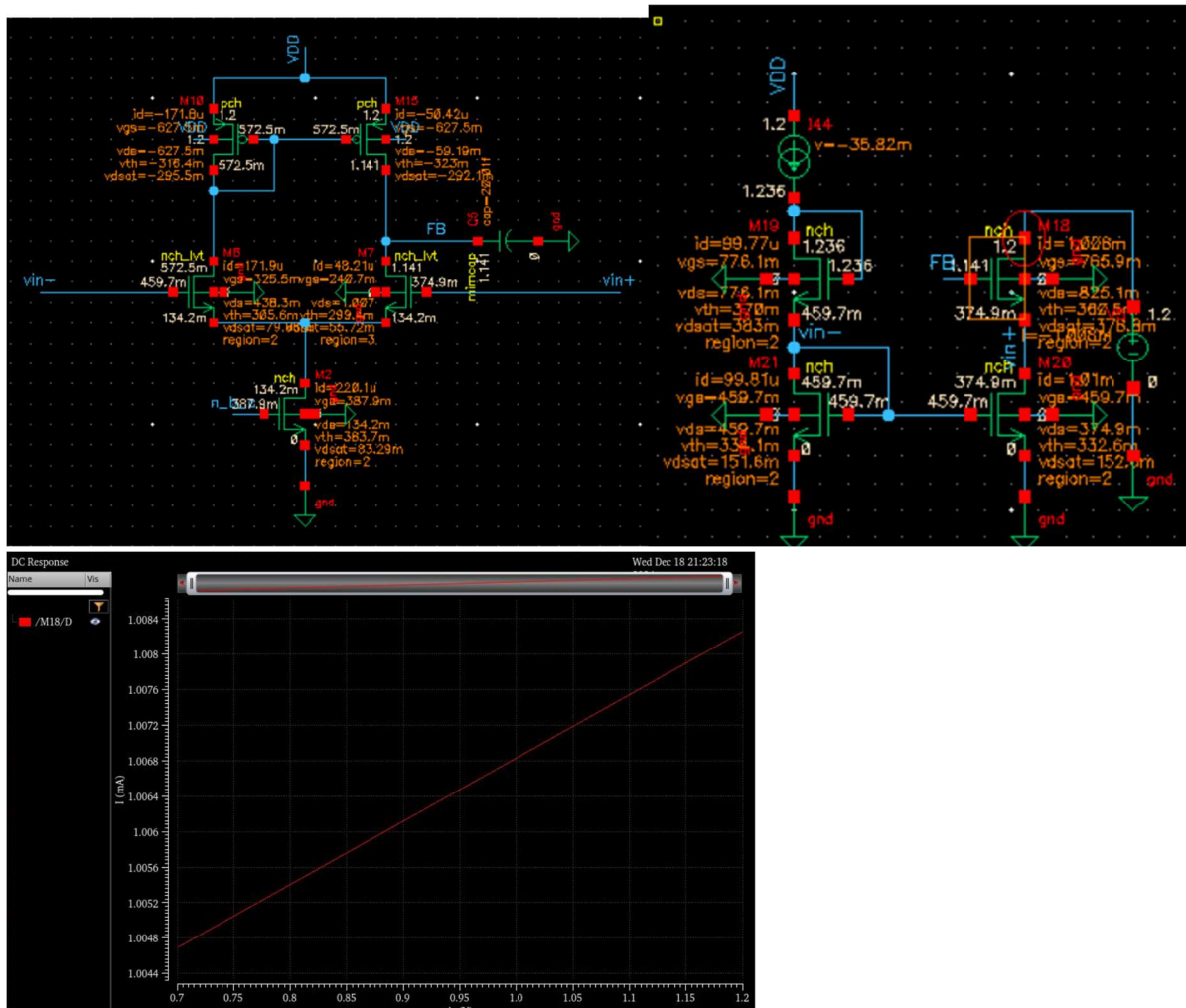

$$I_{1.2V} - I_{0.7V} = 1.00825 - 1.00469 = 0.00356 \text{ mA}$$

$$0.00356 / 1.00469 * 100\% = 0.354\% \text{ variation observed at the current via M18.}$$